

Indian Institute of Technology Hyderabad (IITH)
Electrical Machines Laboratory, Department of Electrical Engineering

Experiment-1: OC, SC and Load Tests on 1- ϕ Transformer

1. Aim of this Experiment

The objective of this experiment is to determine the values of R , X , B_m , and G_i through short circuit and open circuit test as well as to verify the equivalent circuit representation through a load test.

2. Circuit Description and Test Arrangement

The equivalent circuit of a 1- ϕ transformer in approximate form is shown in Figure 1. Here, R and X are the total resistance and leakage reactance respectively of the transformer windings referred to a particular side. Similarly, B_m and G_i are the magnetizing susceptance and the iron loss conductance, respectively, referred to a particular side.

The circuit arrangements for open circuit test, short circuit test, and load test are shown in Figures 2, 3 and 4, respectively.

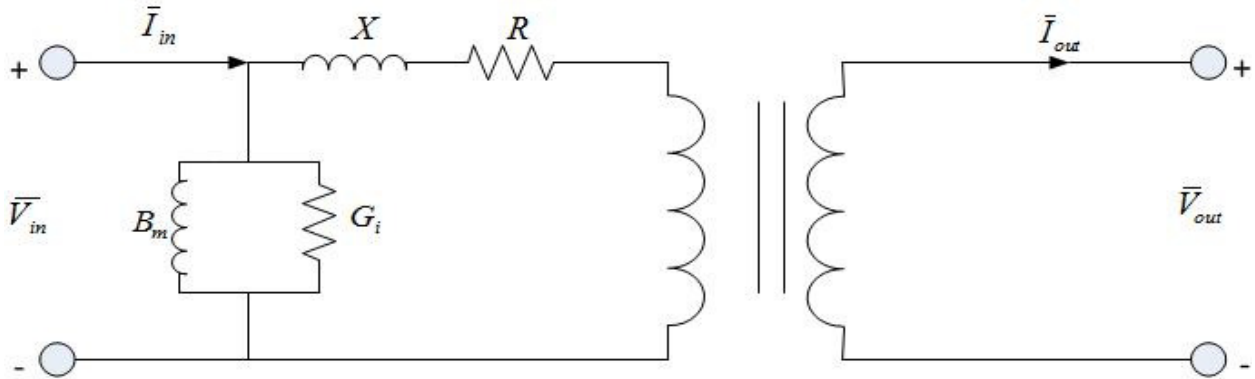


Figure 1. Equivalent circuit representation of a 1- ϕ transformer.

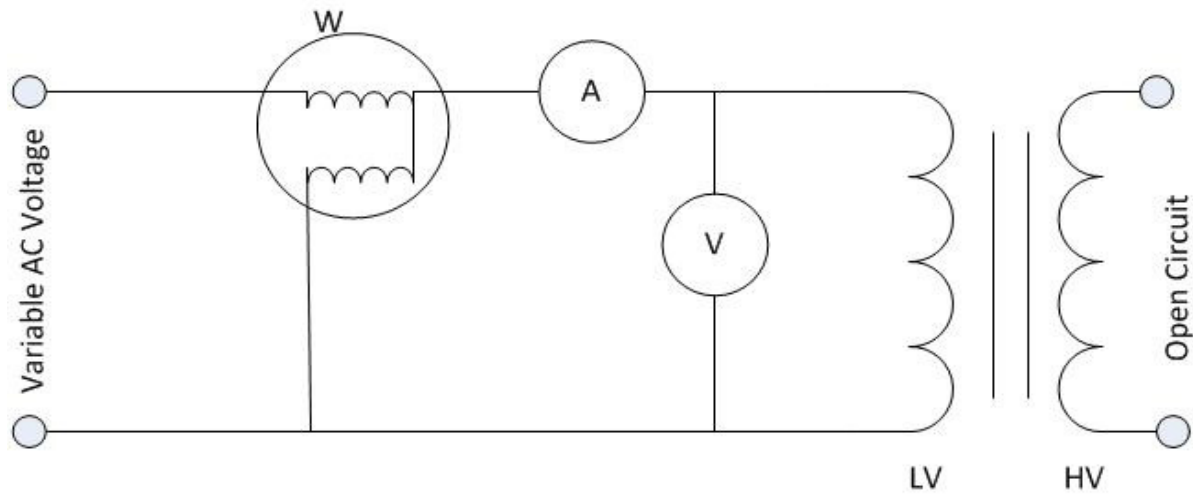


Figure 2. 1- ϕ transformer open circuit test arrangement.

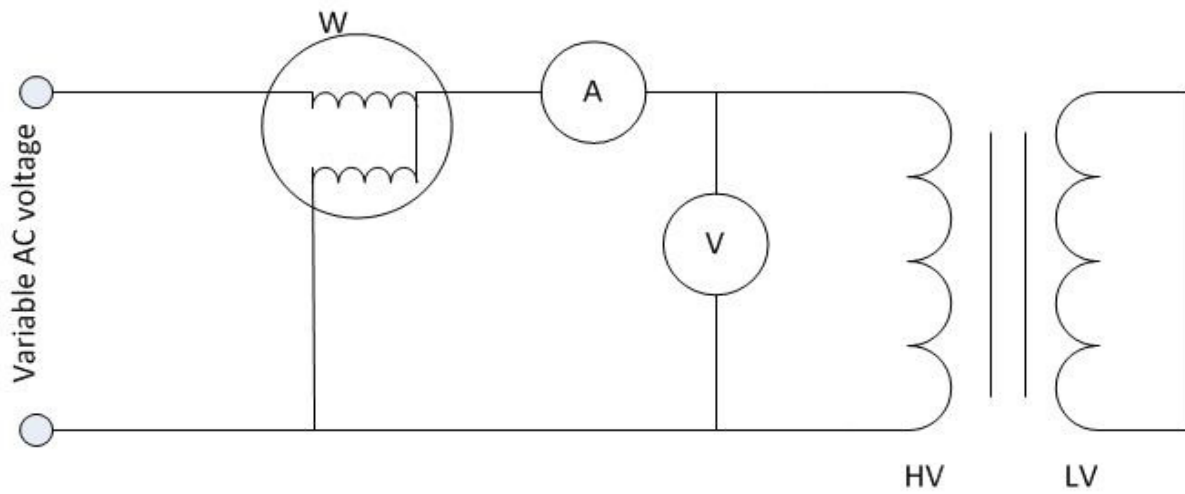


Figure 3. 1- ϕ transformer short circuit test arrangement.

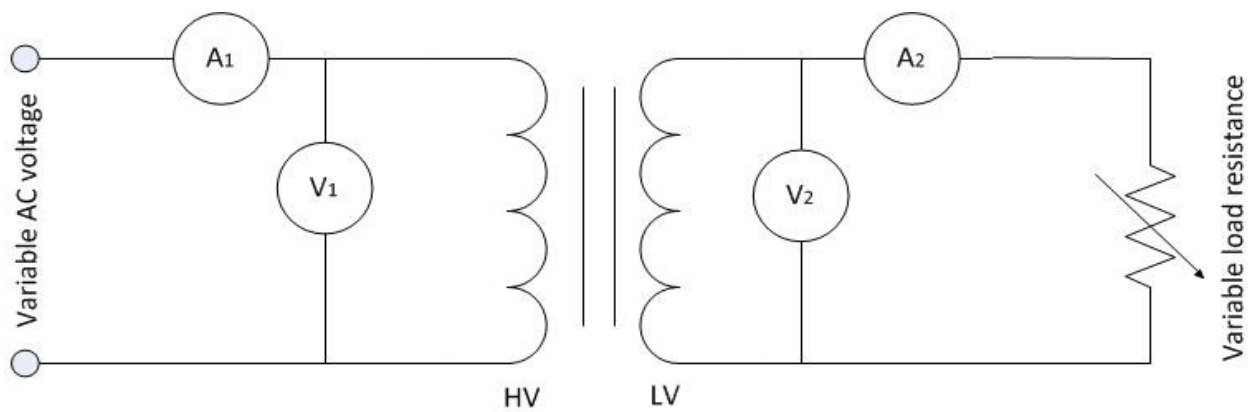


Figure 4. 1- ϕ transformer load test arrangement.

3. Test Procedure

OPEN CIRCUIT TEST:

- Apply rated voltage on the LV side.
- Note down the voltmeter, ammeter, and wattmeter readings (indicated by V_{oc} , I_{oc} and P_{oc} , respectively).
- Determine G_i and B_m (referred to the LV side) by using the following formulae.

$$G_i = \frac{P_{oc}}{V_{oc}^2} \quad (1.1)$$

$$Y = \frac{I_{oc}}{V_{oc}} \quad (1.2)$$

$$B_m = \sqrt{Y^2 - G_i^2} \quad (1.3)$$

SHORT CIRCUIT TEST:

- Establish rated current on the HV side by adjusting the input voltage.
- Note down the voltmeter, ammeter, and wattmeter readings (indicated by V_{sc} , I_{sc} and P_{sc} , respectively).
- Determine R and X (referred to the HV side) by using the following formulae.

$$R = \frac{P_{sc}}{I_{sc}^2} \quad (1.4)$$

$$Z = \frac{V_{sc}}{I_{sc}} \quad (1.5)$$

$$X = \sqrt{Z^2 - R^2} \quad (1.6)$$

LOAD TEST:

- Apply rated voltage on the HV side.
- Take the voltmeter and ammeter readings (indicated by V_{L1} , V_{L2} , I_{L1} and I_{L2}) for different settings of the resistance bank.
- For a particular setting of the resistance bank, the value of load resistance (indicated by R_L) can be found from the readings of Voltmeter 2 and Ammeter 2.
- For a given value of load resistance and input voltage, calculate the value of I_{L1} from the equivalent circuit.

4. Results and Discussions

OPEN CIRCUIT TEST:

$$V_{oc} = \quad G_i \text{ (referred to LV side)} = \quad B_m \text{ (referred to LV side)} =$$

$$I_{oc} = \quad G_i \text{ (referred to HV side)} = \quad B_m \text{ (referred to HV side)} =$$

$$P_{oc} =$$

SHORT CIRCUIT TEST:

$$V_{sc} = \quad R \text{ (referred to HV side)} = \quad X \text{ (referred to HV side)} =$$

$$I_{sc} = \quad R \text{ (referred to LV side)} = \quad X \text{ (referred to LV side)} =$$

$$P_{sc} =$$

LOAD TEST:

V_{L1} (measured)	V_{L2} (measured)	I_{L1} (measured)	I_{L2} (measured)	R_L (calculated)	I_{L1} (calculated)

5. Conclusions

Comment on the accuracy of the equivalent circuit representation.
