

## Experiment - 1 (EE19BTECH11041)

Aim:-


The Objective of this experiment is to determine the values of  $R$ ,  $X$ ,  $B_m$ ,  $G_i$  through short circuit and open circuit test as well as to verify the equivalent circuit representation through load test.

Procedure:-

Open Circuit test:-

- ① Apply rated voltage on the LV side.
- ② Note down the Voltmeter, ammeter and wattmeter reading (indicated by  $V_{oc}$ ,  $I_{oc}$  and  $P_{oc}$ , respectively.)
- ③ Determine  $G_i$  and  $B_m$  (LV side) by using the formula

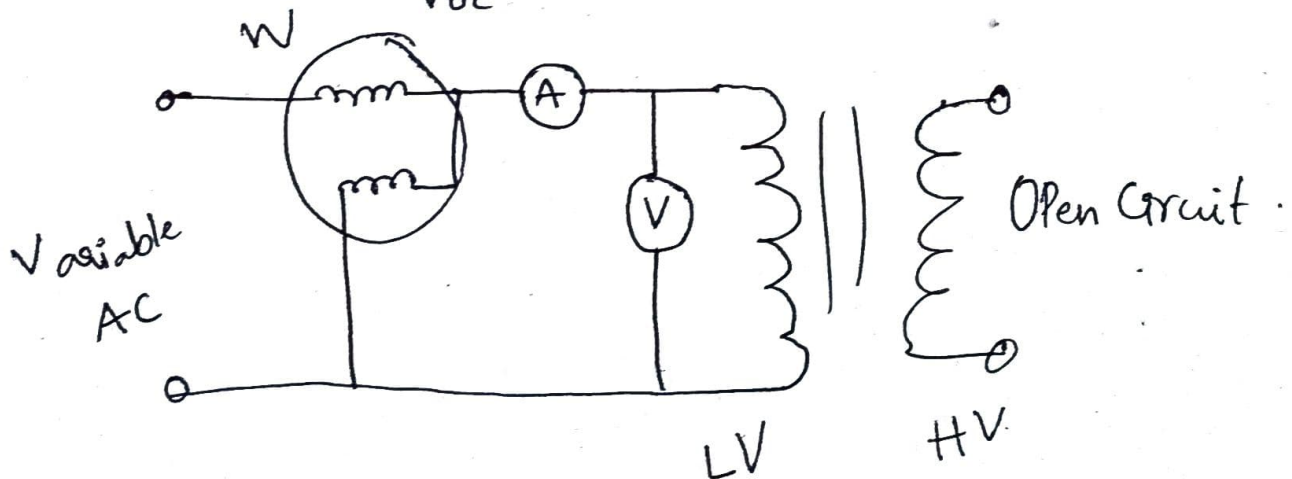
$$G_i = \frac{P_{oc}}{V_{oc}^2}, \quad Y = \frac{I_{oc}}{V_{oc}}, \quad B_m = \sqrt{Y^2 - G_i^2}$$


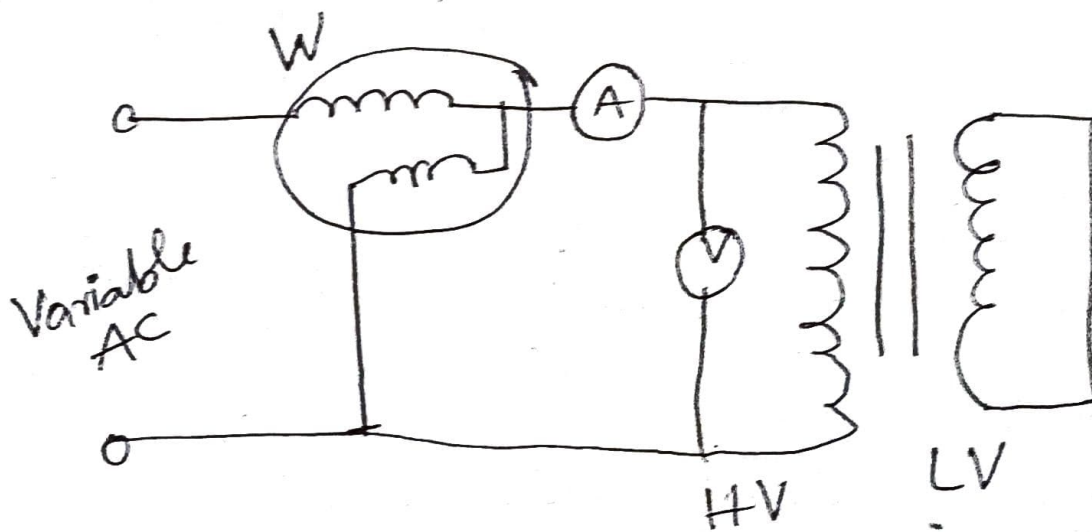
## Short Circuit Test

- ① Establish rated current on the HV side by adjusting the input voltage.
- ② Note down the Voltmeter, ammeter and wattmeter reading (indicated by  $V_{sc}$ ,  $I_{sc}$  and  $P_{sc}$ , respectively)
- ③ Determine  $R$  and  $X$  (HV side) by using the formulae.


$$R = \frac{P_{sc}}{I_{sc}^2}, \quad Z = \frac{V_{sc}}{I_{sc}}, \quad X = \sqrt{Z^2 - R^2}$$



1- $\phi$  transformer SC test
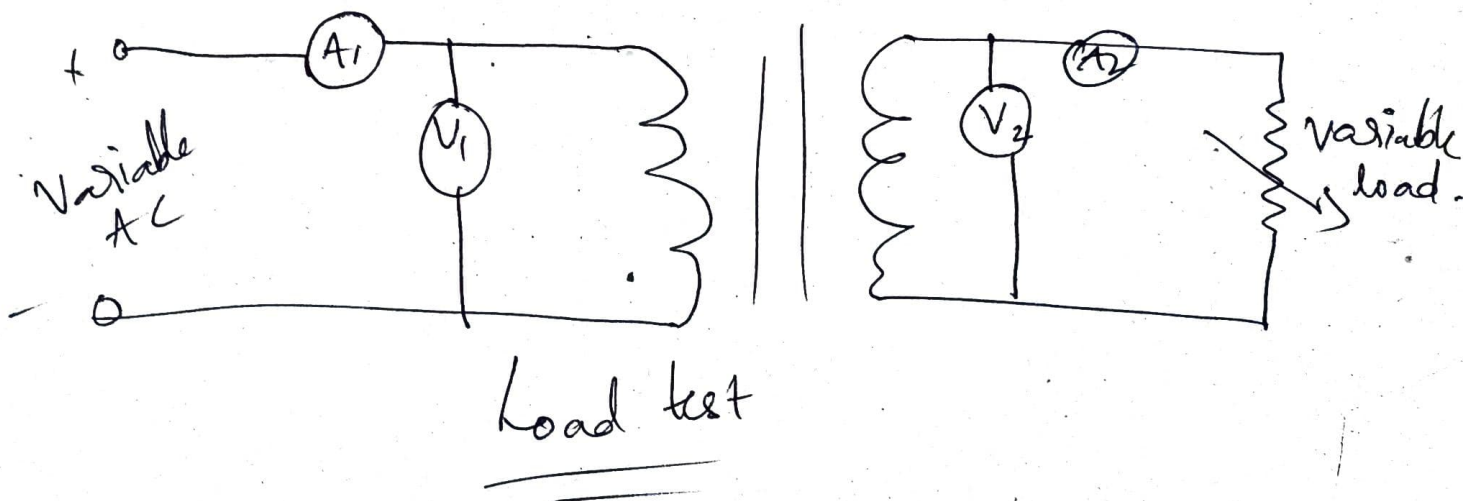
## Load test:

- ① Apply rated voltage on LV/HV side.
- ② Take the Voltmeter and Ammeter readings for different settings of the resistance Bank.
- ③ For a particular setting of the resistance bank, the value of load resistance can be found from the reading of Voltmeter 2 and Ammeter 2.
- ④ For a given value of load resistance and input voltage, calculate the value of  $I_{L1}$  from the equivalent circuit.



## Results and Observations:

### Open circuit test:

$$V_{oc} = 120V$$

$$G_i = \frac{P_{oc}}{V_{oc}^2} = \frac{11}{(120)^2} = 0.00076 \text{ (LV)}$$

$$I_{oc} = 0.20A$$

$$P_{oc} = 11W$$

$$Y = \frac{I_{oc}}{V_{oc}} = \frac{0.2}{120} = 0.00167 \text{ (LV)}$$

$$B_m = \sqrt{Y^2 - G_i^2} = 1.48 \times 10^{-3}$$

$$\boxed{B_m = 0.00148 \text{ (LV)}}$$

### Short circuit test:

$$G_i(HV) = G_i(LV) \times \frac{1}{a^2} = \frac{1}{4} \times G_i = 0.00019 S$$

$$Y(HV) = Y(LV) \times \frac{1}{a^2} = 0.0004175 S$$

$$B_m(HV) = B_m(LV) \times \frac{1}{a^2} = 0.00037 S$$



## Short circuit test

$$V_{sc} = 12V$$

$$I_{sc} = 2.19A$$

$$P_{sc} = 24W$$

$$R(HV) = \frac{P_{sc}}{I_{sc}^2} = \frac{24}{(2.19)^2} = 5.004 \Omega$$

$$Z(HV) = \frac{V_{sc}}{I_{sc}} = \frac{12}{2.19} = 5.4795 \Omega$$

$$X = \sqrt{Z^2 - R^2} = 2.2326 \Omega$$


$$R(LV) = R(HV) \times \frac{1}{a^2} = 5.004 \times \frac{1}{4} = 1.251 \Omega$$

$$Z(LV) = Z(HV) \times \frac{1}{a^2} = 5.4795 \times \frac{1}{4} = 1.3698 \Omega$$

$$X(LV) = X(HV) \times \frac{1}{a^2} = 2.2326 \times \frac{1}{4} = 0.55815 \Omega$$
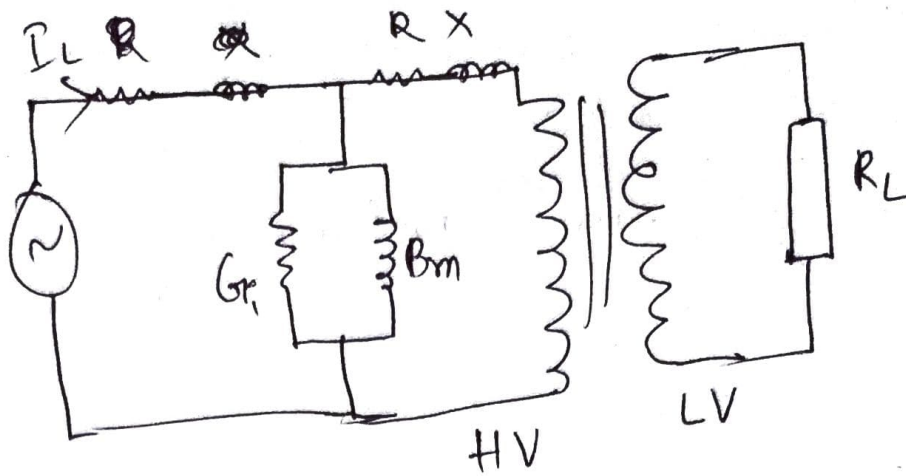
## Load test

Values observed. let's say  $V_1, I_1, V_2, I_2$



$$R_L = \frac{V_2}{I_2} \quad , \quad R_L' = R_L \times a^2$$

(LV)                      (HV) =  $\frac{V_2}{I_2} \times 4$

$$I_{L1} = \frac{V_{L1}}{\left( (R + R_L' + jX) \parallel (G_i \parallel B_m) \right)}$$

$$= \frac{V_{L1}}{\underbrace{(R + R_L' + jX)}_Z \parallel \underbrace{\left( \frac{1}{G_i - jB_m} \right)}_{Y_0}}$$

$$I_{L1} = \left( \frac{V_{L1}}{\frac{Z}{Y_0}} \right) \frac{1}{1 + Z Y_0}$$

# Load test

$$R_L = \frac{V_2}{I_2}$$

$$I_{L1} = \frac{\frac{V_{L1}}{\frac{Z}{Y_0}}}{\frac{1}{Y_0} + Z}$$

$$Z = R + R_L' + jX$$

$$Y_0 = G_0 - jB_m$$

$V_{L1}$	$I_{L1}$	$V_{L2}$	$I_{L2}$	$R_L$ (calculated)	$I_{L1}$ (calculated)
$\frac{400}{\sqrt{3}}$	0.67	121	1.17	103.4 $\Omega$	0.601 A
$\frac{400}{\sqrt{3}}$	0.73	120	1.29	93.02	0.662 A
$\frac{400}{\sqrt{3}}$	0.93	120	1.70	70.5 $\Omega$	0.85 A
$\frac{400}{\sqrt{3}}$	1.3	118	2.39	49.37 $\Omega$	1.18 A
$\frac{400}{\sqrt{3}}$	2.15	116	4.03	28.78 $\Omega$	1.96 A

### Precautions:

- ① Before doing the experiment we should check the fuse.
- ② we need to be careful to slowly increase voltage rather than suddenly.
- ③ Same applies to load resistance.

### Comments:

According to load test we can see that there is an  $0.05\text{ A}$  error when measured and calculated. This may be due to any number of causes.